

# K map for Boolean Expression

Ballepu dheeraj kumar

September 12, 2022

## Contents

### 1 Components

### 2 Hardware

### 3 Software

#### Abstract

This manual shows how to use Arduino uno and LED to represent the boolean expression.

## 1 Components

Components	Value	Quantity
Arduino	UNO	1
LED	-	1
Jumper wires	M-M	3
Breadboard		1

## 2 Hardware

**Problem 2.1** Make connections between the Arduino and LED using Breadboard.

## 3 Software

**Problem 3.1.** execute the following program after downloading.

<https://github.com/ballepu1994>

	U	V	W	Z	G
1	0	0	0	0	0
1	0	0	0	1	0
	0	0	1	0	0
1	0	0	1	1	1
	0	1	0	0	0
	0	1	0	1	1
	0	1	1	0	1
	0	1	1	1	1
	1	0	0	0	0
	1	0	0	1	0
	1	0	1	0	0
	1	0	1	1	1
	1	1	0	0	1
	1	1	0	1	1
	1	1	1	0	0
	1	1	1	1	1

Truth Table

		WZ			
		00	01	11	10
UV	00	0	0	1	0
	01	0	1	1	1
	11	1	1	1	0
	10	0	0	1	0

### K-Map

U, V, W, Z are the inputs and LED is the output. Using boolean logic.

$$A = WZ + VZ + UVW' + U'VW \quad (1)$$